

Current Mirrors/Active Loads

Overview

- Current mirrors
- Active loads
- Voltage and current references


Current Mirrors

➤ Desired features

- Generate an output current equal to input current multiplied by desired current gain factor
- Current gain is independent of input frequency
- Output current independent of output voltage to common node
- Input voltage to be zero to let a larger voltage appear across input current source

➤ In reality

 - Variation of output current with voltage change at output => increase output resistance in small signal
- Deviation of current gain from ideal number
- V_{in} is a finite number that need to be minimized




Simple Bipolar Current Mirror

- Simplest form of current mirror
- Operation
 - Diode connecting base to collector in Q1, operation in active mode
 - $V_{be1} = V_{be2}$

$$I_{C2} = \frac{I_{S2}}{I_{S1}} I_{C1}$$

 - Writing KCL for point 1
- Current gain defined by saturation current => emitter areas
- Systematic error source
 - ☛ β_F




$$I_{IN} - I_{C1} - \frac{I_{C1}}{\beta_F} - \frac{I_{C2}}{\beta_F} = 0$$

$$I_{OUT} = \frac{I_{S2}}{I_{S1}} I_{IN} \left(\frac{1}{1 + \frac{1 + I_{S2}/I_{S1}}{\beta_F}} \right) \xrightarrow{I_{S1} = I_{S2}} I_{OUT} \sim I_{IN}$$

Simple Bipolar Current Mirror (cont.)

 
- In case of finite output resistance, change of output voltage changes I_{C2}
- Output current



$$I_{OUT} = \frac{I_{S2}}{I_{S1}} I_{C1} \left(1 + \frac{V_{CE2} - V_{CE1}}{V_A} \right) = \frac{\frac{I_{S2}}{I_{S1}} I_{IN} \left(1 + \frac{V_{CE2} - V_{CE1}}{V_A} \right)}{1 + \frac{1 + I_{S2}/I_{S1}}{\beta_F}}$$


Simple MOSFET Current Mirror

 - Simple current source
- Operation
 - M1, diode connected, operates in saturation
 - $V_{gs2} = V_{gs1}$
 - The current gain is defined by device sizes
 - Error source



Beta Helper

 - Adding another transistor to reduce the β_f source of error
 - Common for PNP that has lower β_f
- Features
 - Does not change output resistance or output voltage from simple bipolar current mirror
 - Increases the input voltage by another base-emitter voltage
 - Can be used for multiple output current sources



If Q_1 & Q_3 identical

$$\Rightarrow I_{OUT} = I_{IN} \left(1 - \frac{2}{\beta_F(\beta_F + 1)} \right)$$

Cascode Current Mirror

Simple case

- Achieves very high output gain

- Each cascode stage increases the output resistance by $(1+g_m r_o)$

$$R_o = r_{o2} [1 + (g_{m2} + g_{mb2}) r_{o1}] + r_{o1}$$

- Minimum input voltage:


- For each stage, we add one $(V_t + V_{ov})$ to this minimum
 - Challenge for low voltage design

$$V_{IN(\min)} = 2V_t + 2V_{ov}$$

- Minimum output voltage:

- So V_{DS1} is a threshold voltage more than it needs to be


$$V_{Out(\min)} = V_t + 2V_{ov}$$

 

Cascode Current Mirror Improved Voltage Swing

- In order to improve the output swing, we need to voltage shift the gate voltage of M2
 - In case we use same transistors for all the devices $\Rightarrow V_{DS1}=0$
 - So we need to find optimum dimensions to give $V_{DS1}=V_{ov}$
- Output resistance is similar to simple cascode
- The input voltage is worsened
- The systematic gain error worsened, since M1 & M3 form a current mirror with unequal drain-source voltages
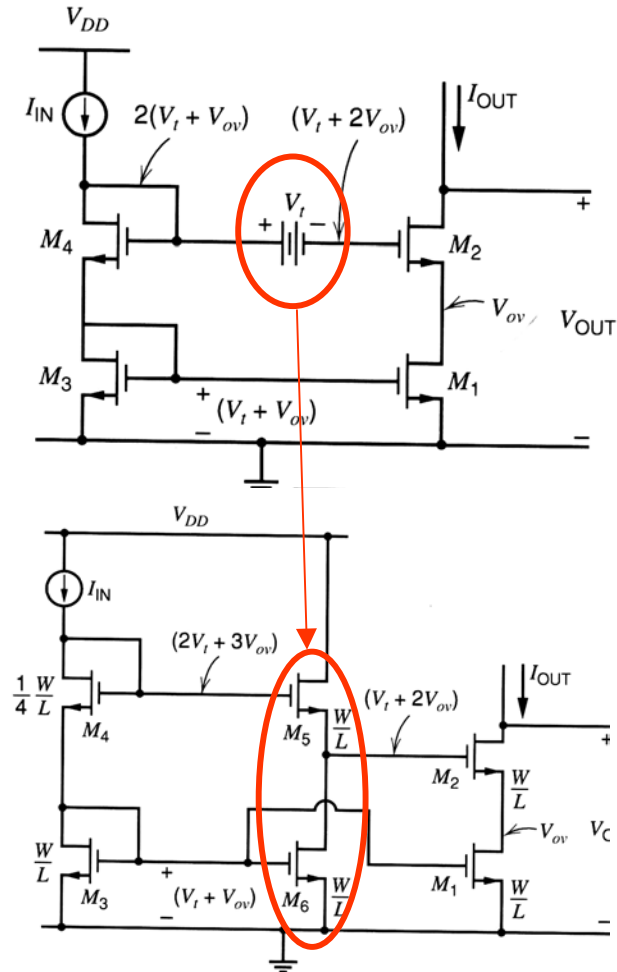
$$\varepsilon = \frac{V_{DS1} - V_{DS3}}{V_A} \approx \frac{V_{ov1} - (V_{ov1} + V_t)}{V_A} = -\frac{V_t}{V_A}$$



Cascode Current Mirror

Sooch Cascode

- To improve on mismatch and some power consumption, we could fold the level shift into one transistor
- The output resistance:

$$R_o = r_{o2} [1 + (g_{m2} + g_{mb2})r_{o1}] + r_{o1}$$


- Minimum input voltage:

$$V_{IN(\min)} = 2V_t + 3V_{ov}$$

- Minimum output voltage:

$$V_{OUT(\min)} \approx V_t + 2V_{ov}$$

 - M4 ensures Q1 & Q3 have same VDS => systematic gain error goes to zero



Cascode Current Mirror


Low Voltage Cascode

- For many low voltage applications, it is important to reduce the input voltage of cascode; this can be achieved by splitting the input branches
- Two input voltages need to satisfy:

$$V_{IN1(\min)} = V_t + 2V_{ov}$$

$$V_{IN2(\min)} = V_t + V_{ov}$$

 - Therefore can be achieved with lower supply voltages



Wilson Current Source

- Goal is reducing the systematic error and achieve large output resistance

- The output resistance is given by:

$$R_o = r_{o2} [2 + g_{m2} r_{o3}]$$


- Minimum input voltage:

$$V_{IN(\min)} = 2V_t + 2V_{ov}$$

- Minimum output voltage:

$$V_{OUT(\min)} \approx V_t + 2V_{ov}$$

 - Systematic error is zero, since $V_{DS1} = V_{DS3}$





Active Loads

- To achieve a high gain
 - Need large load resistance
 - Difficult to realize resistor in an integrated circuit
 - But it is much cheaper/easier to use resistors => Active load
- Configurations
 - Common source with complementary load
 - Common source with diode load
 - Differential pair with current mirror load

Common Source with MOS Load

- In this case, T2 operation is mostly defined by T3
- Output voltage is given by: $V_{OUT} = V_{DD} + V_{ds2}$
- In most part, the gain is not linear. But we can bias it in a narrow regime that gain stay constant for short channel devices
  
$$\frac{V_{OUT}}{V_{IN}} = -g_{m1}(r_{o1} \parallel r_{o2})$$



Common Source with Diode Connected Load



- In this case, the load resistance is proportional to $1/g_{m2}$
- Large signal analysis shows that the circuit is operational for

- V_{in} greater than one threshold voltage
- V_{out} could only go to $(V_{DD} - V_{t2})$

- Small signal gain:

$$V_o = V_{DD} - V_{t2} - \sqrt{\frac{(W/L)_1}{(W/L)_2}} (V_i - V_{t1})$$
  
$$\frac{v_o}{v_i} = -\sqrt{\frac{(W/L)_1}{(W/L)_2}}$$



Differential Pair with Active Load (cont.)

- An alternative circuit is shown here:

- Turning a differential pair into single ended

- Investigating small signal model shows the transconductance of actively loaded Diff-Pair is twice of resistively loaded



$$G_m = g_{m(dp)} = g_{m1}$$

- The output resistance

$$R_o = r_{o2} \parallel r_{o4}$$

- Large output resistance, requires next stage also has a large input resistance

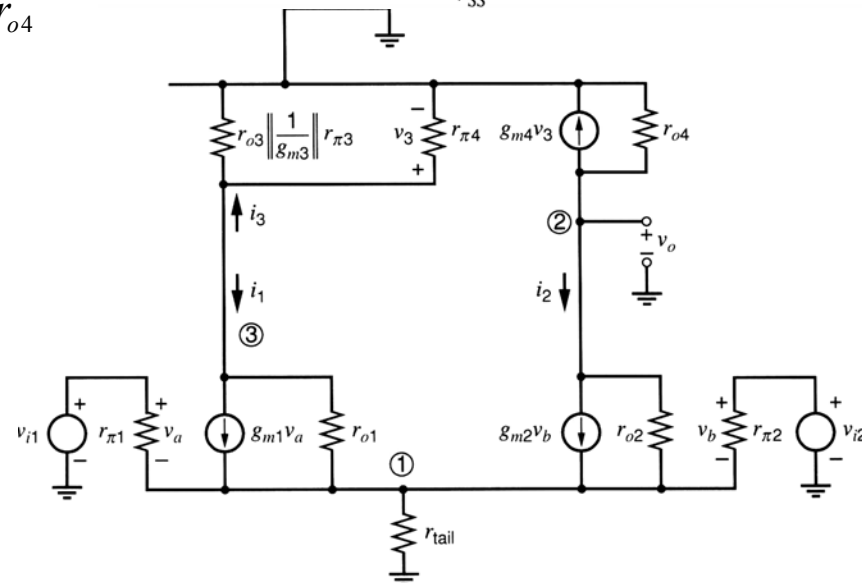 - Active load also improves CMRR by a factor of $2g_{m1}(r_{o2} \parallel r_{o4})$




Voltage and Current Sources

- Low current biasing techniques for achieving small bias currents
 - Widlar current source
 - Peaking current source
- Supply insensitive biasing
 - Self biasing
- Temperature insensitive biasing
 - Band gap referenced circuit

Mos Widlar Current Sources

- Similar to Widlar current mirror, but addition of resistor makes output current less dependent of input current
- Output current depends on input current and resistor R_2
 
$$\sqrt{I_{out}} = \frac{-\sqrt{\frac{2}{k'(W/L)_2}} + \sqrt{\frac{2}{k'(W/L)_2} + 4R_2V_{ov1}}}{2R_2}$$




MOS Peaking Current Source

- To achieve even lower current values, the size of resistors will grow fast; alternatively we could use this class of circuits
- The output current is given;

- In saturation:
$$I_{out} = \frac{k'(W/L)_2}{2} (V_{ov1} - I_{in}R)^2$$

 - In sub-threshold:
$$I_{out} \approx I_{in} \exp\left(-\frac{I_{in}R}{nV_T}\right)$$






Supply Insensitive Biasing

- An important aspect in a design is sensitivity to biases
 - Defined by:

$$S_{V_{SUP}}^{I_{OUT}} = \frac{V_{SUP}}{I_{OUT}} \frac{\partial I_{OUT}}{\partial V_{SUP}}$$


- Self biasing uses the concept of positive feedback; the input current is directly related to output current
- Needs an startup circuit to avoid zero current case
- A common approach is V_T referenced self-bias circuit

$$I_{out} = V_T \frac{\ln(n)}{R}$$

 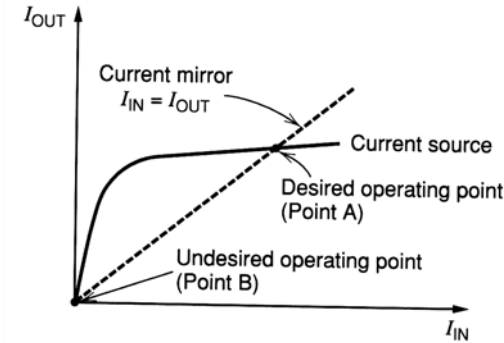 

Temperature Insensitive Biasing

 - Designing temperature independent references
 - Band-gap referenced
- Using parasitic BJT in CMOS process, we can design band-gap referenced circuit



$$V_{out} = V_{EB2} + \left(1 + \frac{R_2}{R_3}\right) \Delta V_{EB} + \left(1 + \frac{R_2}{R_3}\right) V_{OS}$$

$$\Delta V_{EB} = V_T \ln \left(\frac{I_1 I_{S2}}{I_2 I_{S1}} \right)$$

Summary

- Sources and current mirrors
- Using active loads instead of plain resistors
- Temperature and bias insensitive circuits
- Practice questions: 4-5, 4-10, 4-12, 4-23, 4-25